

B.Sc. Sem.-6 Examination

CC - 307

Electronics

July 2021

Time : 2-00 Hours]

[Max. Marks : 50

- Instructions: (1) All questions in Section-I carry equal marks
 (2) Attempt any Three questions in Section – I.
 (3) Question – 9 in section – II is compulsory

SECTION - I

- Q-1 (A) Draw the circuit of Op-Amp log amplifier using transistor as feedback element and derive necessary equation for output voltage. 7
 (B) Describe the application of Op-Amp as an integrator and obtain expression of output voltage. Also draw frequency response of the integrator circuit. 7
- Q-2 (A) Describe the application of Op-Amp comparator as zero crossing detectors. 7
 (B) Write a short note on regenerative comparator using Op-Amps. 7
- Q-3 (A) Draw the block diagram of PLL and explain basic principle of PLL. 7
 (B) Explain the application of EX-OR gate in digital phase detector. 7
- Q-4 (A) Explain the application of PLL as AM detector 7
 (B) Write a short note on Edge-Triggered phase detector using NOR gates. 7
- Q-5 (A) Explain the working of SCR using two transistor analogies. 7
 (B) Explain the terms used for SCR (1) PRV (2) holding current (3) forward current rating 7
- Q-6 (A) Write a short-note on Forced commutation of an SCR. 7
 (B) A half wave rectifier circuit employing an SCR is adjusted to have a gate current of 1mA. The forward breakdown voltage of SCR is 100V for $I_g=1\text{mA}$. If a sinusoidal voltage of 200V peak is applied, find: (1) firing angle (2) conduction angle (3) average current. Assume load resistance = 100Ω and the holding current to be zero. 7
- Q-7 (A) Explain the operation of TRIAC in different possible modes. 7
 (B) Write a short note on TRIAC phase control circuit. 7
- Q-8 (A) Explain the application of UJT in the relaxation oscillator. 7
 (B) In a basic UJT relaxation oscillator circuit, $R_1=33\Omega$, $R_2=330\Omega$, $\eta=0.54$, $C=0.2\mu\text{F}$, a variable resistor R_E (between positive terminal of V_{in} and emitter) is used to change the frequency of pulses delivered at V_{out} . The variable resistor is initially set at $5\text{k}\Omega$ and is then adjusted to $10\text{k}\Omega$. Determine the frequency of the voltage spikes produced for (1) $5\text{k}\Omega$ setting and (2) $10\text{k}\Omega$ setting. 7

SECTION - II

- Q-9 Attempt ANY EIGHT. (Each question carry 1 mark) 8
- 1 What is 'virtual ground'?
 - 2 Write the names of any two applications of analog multipliers?

PTO

M 93-2

- 3 Draw the basic circuit of voltage to current converter using Op-Amp.
 - 4 Why temperature compensation is required for basic Op-Amp log amplifier?
 - 5 Enlist any two applications of PLL?
 - 6 Enlist any two building blocks of PLL.
 - 7 What is the full form of VCO?
 - 8 What is the function of LPF in PLL?
 - 9 From which semiconductor, the SCR is made of?
 - 10 Draw the symbol of SCR.
 - 11 Write any one advantages of SCR as switch over a mechanical switch.
 - 12 What is the full form of SCR?
 - 13 How many semiconductor layers does the schematic of DIAC have?
 - 14 What is the advantage of the TRIAC over the SCR?
 - 15 How many junction/junctions a UJT has?
 - 16 Draw the symbol of TRIAC.
-