

**BC-102**

May-2015

**B.Sc., Sem.-IV**

**CC-204 : Electronics**

**Time : 3 Hours]**

**[Max. Marks : 70**

- Instructions :** (1) All questions carry equal marks.  
(2) Symbols used here have their usual meanings.

1. (a) What is the role of feedback network in RC oscillators ? Discuss the RC phase-shift oscillator in detail. 7

**OR**

Differentiate between the Colpitt's and Hartley oscillators circuit. Draw the circuit of Hartley oscillator and explain its working.

- (b) List the types of multi-vibrators and explain transistorized bistable multi-vibrator in detail. 7

**OR**

A rectangular pulse of voltage is applied to the base of a transistor driven into heavy saturation. Explain different switching times in a transistor with the help of waveforms.

2. (a) Prove that the optimum conversion efficiency in pure class-B push-pull amplifier circuit is 78.5%. 7

**OR**

What disadvantages are there in a single ended transformer coupled power amplifier ? Explain the transformer saturation.

- (b) What principal factor contributes to the doubling of the conversion efficiency in a transformer coupled load amplifier compared with an amplifier with a direct coupled resistive load ? What other advantages does the transformer provide ? 7

**OR**

Explain cross-over distortion. What it is caused by, and how it is overcome ?

3. (a) List the basic processes used in silicon planar technology. Write a note on photolithography. 7

**OR**

Explain the method used for fabricating diffused type IC resistor. Give the dimensions of a 4000  $\Omega$  defused resistor.

- (b) Discuss the various ways for fabricating pnp transistors. 7

**OR**

Explain importance of SiO<sub>2</sub> layer. How thick is this layer ?

4. (a) Draw the circuit diagram of inverting amplifier. Prove  $A_{CL} = -R_f/R_1$  for inverting OP-AMP. Design an amplifier with a gain of -10 and input resistance equal to 10 kΩ. 7

**OR**

Describe the terms (1) input bias current (2) input offset current (3) input offset voltage (4) thermal drift.

- (b) For non inverting amplifier prove  $A_{CL} = 1 + (R_f/R_1)$ . What is voltage follower ? 7

**OR**

A square wave of peak-to-peak amplitude of 500 mV has to be amplified to peak-to-peak amplitude of 3 volts, with a rise time of 4 μs. Calculate slew rate. Can a 741 be used ?

5. Answer in short : 14

- (1) What disadvantage does a phase-shift oscillator have ?
- (2) Where resonant type oscillators are used ?
- (3) An astable multi-vibrator has component values  $R_{B1} = R_{B2} = R = 10 \text{ k}\Omega$ , and  $C_1 = C_2 = C = 120 \text{ pF}$  and  $R_{L1} = R_{L2} = R_L = 1 \text{ k}\Omega$ . Find frequency of oscillation.
- (4) How many stable states does an astable multi-vibrator have ?
- (5) What type of bias is used in a true class B push-pull amplifier ?
- (6) What are the advantages does push-pull provide ?
- (7) The maximum theoretical conversion efficiency of a class A amplifier utilizing a direct coupled resistive load is \_\_\_\_\_.
- (8) Give any two advantages of integrated circuits over the circuits those made by interconnecting discrete components.
- (9) What is the full form of SiO<sub>2</sub> ?
- (10) What is VLSI ?
- (11) Why n-p-n transistors are preferred in integrated circuits compared to p-n-p transistors ?
- (12) Define slew rate ?
- (13) What is the full form of DIP ?
- (14) A 741 op amp is available in a 14-pin DIP package. What is the pin number for (1) inverting input (2) non-inverting input (3) output