

Seat No. : \_\_\_\_\_

**DA-110**  
**December-2013**  
**B.Sc. Sem.-V**  
**ELE-303 : Electronics**

**Time : 3 Hours]**

**[Max. Marks : 70**

- Instructions :**
- (1) **All** questions carry equal marks.
  - (2) Symbols and terminology used here have their usual meanings.
  - (3) Internal options are given in Q-1, 2, 3 and 4.
  - (4) Q-5 is compulsory.
  - (5) Scientific calculator is allowed.
  - (6) Mobile phones are strictly prohibited during exam time.
  - (7) Attempt **all** questions.

1. Draw and discuss the “Chopper type DC amplifier Voltmeter” in detail with necessary diagrams. **14**

**OR**

Draw and discuss the “Shunt type Ohmmeter and its calibration with necessary circuit diagrams.

Suppose a Shunt type Ohmmeter uses a 20 mA basic D’Arsonal movement with an internal resistance of  $70 \Omega$ . The battery voltage is 5 V. It is desired to modify the circuit by adding appropriate Shunt resistance across the movement so that the instrument indicates  $30 \Omega$  at the midpoint scale. Calculate

- (1) The value of Shunt resistance
  - (2) The value of Current limiting resistance R1
2. Draw and discuss the “Dual slope integrating type DVM using voltage to Time conversion technique with needed diagrams. **14**

**OR**

Draw and discuss the “Integrating type DVM using Voltage to Frequency conversion technique with needed diagrams.

3. Draw neat and clean block diagram for a general purpose CRO and explain its function in detail. Discuss the CRT circuits with necessary diagram. **14**

**OR**

What is Delay line ? Discuss the function of Delay Line and distributed parameter delay line in detail.

4. Draw and discuss the pulse characteristics and terminology using necessary diagrams. **14**

**OR**

Explain the working and function Laboratory Square wave and Pulse Generator with suitable in detail.

5. Answer the following : (**One** mark each) **14**

- (1) What is Duty cycle ?
  - (2) Define : Rise time.
  - (3) Write the formula for closed loop gain of the feedback amplifier.
  - (4) What is “Graticules” ?
  - (5) Define the deflection sensitivity.
  - (6) Write the full form of SAR.
  - (7) Draw the simple “Sample & hold circuit” clearly.
  - (8) What is propagation delay ?
  - (9) What is TVM ?
  - (10) What is Modulation percentage ?
  - (11) Draw the effect of Overcompensated probe.
  - (12) What is “Fluorescence” ?
  - (13) Define : Persistence.
  - (14) What is “Multi trace” ?
-