

Seat No. : _____

NI-102
November-2013
B.Sc. Sem.-III
ELE-202 : Electronics

Time : 3 Hours]

[Max. Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Symbols used have their meanings as usual.

1. (a) If a T section is interposed between a generator having internal impedance Z_{1i} and a load impedance Z_{2i} , explain image impedance matching giving suitable circuit and show 7

$$Z_{1i} = \sqrt{Z_{1oc} Z_{1sc}} \quad \text{and} \quad Z_{2i} = \sqrt{Z_{2oc} Z_{2sc}}$$

- (b) Explain how magnetically coupled circuit can be replaced by equivalent impedance transforming T network. 7

OR

- (a) Explain reactance L-section for impedance transformation assuming $R < R_{in}$ and show values of C and L for desired R_{in} for L-section are 7

$$C = \frac{1}{WR_{in}} \sqrt{\frac{R_{in}}{R} - 1} \quad \text{and} \quad L = \frac{R}{W} \sqrt{\frac{R_{in}}{R} - 1}$$

R_{in} is desired load for generator

- (b) With necessary circuit explain transformation of impedances using iron core transformer using ideal transformer properties and show, 7

$$Z_{1in} + (R_L + j\omega L_L) \frac{L_1}{L_2} \quad \text{and hence} \quad Z_{1in} + a^2 Z_L.$$

$$a = \text{turns ratio} = \frac{N_1}{N_2}$$

2. (a) What do you understand by wave shaping ? Explain : 3
- (i) Linear wave shaping
- (ii) Non-linear wave shaping
- (b) Give high pass R.C. circuit response to square wave input. 7
- (c) A 10 KHz square wave having $T = 5\mu\text{sec}$ and overall amplitude of 10 volt is applied to a differentiating circuit in which $R = 10\text{ k}\Omega$ and $C = 1000\ \mu\text{F}$. Determine the tip values V_1 , V_2 , V_1^1 and V_2^1 of the output wave form. 4

OR

- (a) What do you understand by filters ? Explain : 6
- (i) neper and
- (ii) decibel
- (b) Suppose output of a network is 2 watt and under changed condition the output is 3.2 watt then by how many decibels will the output change to ? 3
- (c) What is known as symmetrical network ? If a symmetrical T network is terminated into image impedance where characteristic impedance is Z_0 then show 5

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2} \right)}$$

3. (a) Give circuit diagram and truth table for full adder. 7
- (b) Give brief account on Adder-subtractor with necessary diagram. 7

OR

- (a) Give mono-stable operation of timer 555 with functional diagram and explain using timing pulses.

In a monostable multivibrator $R = 100\text{ k}\Omega$ and the time delay $T = 100\text{ ms}$. Calculate value of C. 7

- (b) Give circuit diagram for pulse forming circuit using two monostables 74123. If input to the circuit is 100 KHz square wave and it is desired to produce a $1\ \mu\text{s}$ pulse $2\ \mu\text{s}$ after every positive transition of the input then find out proper timing capacitor values. Given that both timing resistors are set at $500\ \Omega$. 7

4. (a) Give traditional block diagram of a computer and explain function of each block in brief. 7
- (b) Define following terms : 7
- (i) instruction
 - (ii) machine language
 - (iii) assembly language
 - (iv) compiler
 - (v) interpreter
 - (vi) operating system
 - (vii) assembler

OR

- (a) Give five functional categories of 8085 instructions. 7
- (b) Give example of each 7
- (i) 1-byte instruction
 - (ii) 2-byte instruction and
 - (iii) 3-byte instruction

5. Answer the following questions in **one** sentence : 14
- (1) What is meaning of positive edge triggered circuit ?
 - (2) What is dynamic input indicator ?
 - (3) What is meaning of hysteresis when applied to Schmitt trigger ?
 - (4) What is duty cycle ?
 - (5) What are the modes of operation of a timer ?
 - (6) What is full form of ALU ?
 - (7) How many bits are contained in a byte ?

- (8) What is cut off frequency in terms of R and C in case of high pass R-C circuit ?
 - (9) What is a square wave ?
 - (10) Give full form of BCD.
 - (11) Is it true that instruction has two parts op-code and operands ?
 - (12) What do you understand by impedance transformation ?
 - (13) What is Weber-Fechner law ?
 - (14) Two voltages or currents differ by one neper when one of them is e times as large as the other. Is it true ?
-