

Seat No. : \_\_\_\_\_

**JE-107**

**January-2016**

**B.Sc., Sem.-I**

**CC-3 – Paper-101 : Electronics**

**Time : 3 Hours]**

**[Max. Marks : 70**

- Instructions :** (1) All questions carry equal marks.  
(2) Symbols have their own meanings.

1. (a) What is resistor ? Explain its types in detail. Also discuss colour code of resistance. Give the colour code of  $1\text{ m}\Omega \pm 10\%$ . **10**

**OR**

Explain different types of capacitors in detail. What will be the value of capacitance if '103' is written on it ?

- (b) What is the meaning of sensitivity of a voltmeter ? **4**

**OR**

Explain the meaning of loading effect of a d.c. voltmeter using an example.

2. (a) Draw the circuit of diode clamper and explain its working. Also discuss about biased clamper and give its application. **8**

**OR**

Explain about voltage limiter and voltage doubler circuit.

- (b) Write note on: (Any **one**) **6**

(1) Photo diode

(2) LASER diode

3. (a) What is harmonic distortion? Explain about three point method of calculating harmonic distortion. **8**

**OR**

What is "Decibel" ? Which are the other equations for "Decibel computation" ? Also explain about zero decibel reference level.

- (b) Explain the concept of amplification. Give the formula for current, voltage and power gain. **6**

**OR**

Define 'Bel' & 'Decibel'. Explain about the use of a voltmeter as a decibel indicator.

4. (a) Perform 2's complement addition. (Any one) 4  
 (1) 35, -23  
 (2) -78, -11
- (b) Perform 2's complement subtraction. (Any one) 4  
 (1) -39, 27  
 (2) 85, 29
- (c) Convert : (Any one) 4  
 (1)  $A234.56_{(16)} = \text{_____} (2) = \text{_____} (10)$   
 (2)  $953.24_{(10)} = \text{_____} (2) = \text{_____} (16)$
- (d) Perform binary subtraction : (Any one) 2  
 (1) 10101100 - 00111101  
 (2) 11010101 - 01101010
5. Answer the following : 14
- (1) What is the full form of LED ?
  - (2) Define "Clipper".
  - (3) What is shunt ?
  - (4) What would be O/P resistance of an ideal amplifier ?
  - (5) What is ASCII ?
  - (6) What is meant by open circuit ?
  - (7) Define Symmetric network.
  - (8) Define conversion efficiency.
  - (9) Write classes of amplifier operation.
  - (10) Draw the circuit of biased shunt clipper.
  - (11) What is Byte ?
  - (12)  $A \cdot (A + B) = \text{_____}$ .
  - (13) Give 1's complement of 56.
  - (14) Name any two types of 'Relay'.
-