

Seat No. : _____

NN-102
December-2015
B.Sc., Sem.-III
CC-202 : Electronics

Time : 3 Hours]

[Max. Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Symbols have their usual meanings.
(3) Figures to the right indicate marks.

1. (a) Discuss the function of reactance L-section for impedance transformation. Derive the equation for value of L-section reactance for $R > R_g$. 7

OR

Write a note on : Transformation of impedances with tapped resonant circuits.

- (b) Discuss a two-mesh coupled circuit used for impedance transformation. 7

OR

Explain reactance T-networks for impedance transformation in detail.

2. (a) Discuss the response of a low pass RC circuit to a pulse input. 7

OR

Obtain the relation between neper and decibel.

- (b) Explain how a high pass RC circuit behaves as differentiator. 7

OR

Discuss the current and voltage ratio as exponentials in filters

3. (a) Explain Half-adder and Full-adder with the help of Truth Table. 7

OR

Explain how 555 timer can be used as a monostable multivibrator.

- (b) Using full-adders show how to add or subtract binary numbers. 7

OR

Explain how 555 timer can be used as astable multivibrator.

4. (a) Explain Large Computers, Medium-Size Computers & Microcomputers in detail. 7

OR

Explain Machine language, assembly language & high-level language.

- (b) Explain 8085 hardware and programming model in detail. 7

OR

Explain data transfer, arithmetic, logical, branching & machine control operations.

5. Answer in short : 14

1. Define coefficient of coupling.
 2. Draw the equivalent T-Network for ideal transformer.
 3. What is resonance ?
 4. Draw low pass RC circuit.
 5. Draw differentiating circuit.
 6. 1 neper = _____ db
 7. Define filters.
 8. Draw half adder circuit.
 9. What is an ALU ?
 10. Define duty cycle.
 11. List flags of 8085.
 12. What is system bus ?
 13. Define opcode and operand.
 14. Define operating system.
-