

Seat No. : _____

JH-126

June-2022

M.Sc., Sem.-II

410 : Physics

(Analog Electronics – I)

(New Course)

Time : 2 Hours]

[Max. Marks : 50

- Instructions :**
- (1) All questions in Section – I carries equal marks.
 - (2) Attempt any **three** questions in Section – I.
 - (3) Question – 9 in Section – II is COMPULSORY.

Section – I

1. (A) What is Butterworth response ? Discuss first order high pass Butterworth filter. Write different steps for designing such filter. 7
(B) How are filters classified ? What is an all-pass filter ? Where and why is it needed ? 7
2. (A) How IC723 positive voltage regulator works as a foldback current limiter and external current boost transistor ? Discuss. 7
(B) Define Voltage regulation. Explain IC723 high and low voltage regulators with suitable circuit diagram. 7
3. (A) What is poles and zeros in Pole-Zero diagram ? Investigate and explain Pole-Zero diagram of single tuned amplifier and write its use. 7
(B) Obtain expression of bandwidth of tuned secondary FET amplifier with suitable circuit diagram. 7
4. (A) With neat and clean diagram, discuss PLL briefly and clarify lock range and capture range from it. 7
(B) Discuss shunt-peaked video amplifier with maximally flat gain response curve and time delay factor. 7

5. (A) What is power amplifier ? How it differs from a voltage amplifier ? What are the different classes of operation of power amplifiers ? Describe them briefly. 7
- (B) Draw circuit diagram of direct coupled resistive load Class - A power amplifier. Show that the maximum theoretical conversion efficiency of this amplifier is 25 %. 7
6. (A) Draw a circuit diagram of an astable multivibrator using transistors and explain its operation with necessary waveforms. 7
- (B) (i) Write short note on: Cross over distortion 7
- (ii) Discuss advantages and disadvantages of single ended transformer coupled amplifier.
7. (A) Draw basic circuit of a phase shift oscillator using operational amplifier. Sketch the circuit waveforms, and briefly explain the circuit operation. Write the oscillating frequency equation. Discuss the amplifier gain requirements. 7
- (B) Explain application of operational amplifier as Differential bridge amplifier. 7
8. (A) Draw the diagram for an Op-amp integrating circuit. Sketch the output waveforms produced by a rectangular waveform input to the Op-amp integrating circuit. Explain the output waveform. 7
- (B) Explain application of operational amplifier as
- (i) voltage to current converter and
- (ii) current to voltage converter. 7

Section – II

9. Select correct answer from the given options : (Each question is of **ONE** mark) 8
- (i) Sample and hold circuits in analog to digital converters are designed to _____.
- (A) sample and hold the output of the binary counter during the conversion process
- (B) stabilize the comparator's threshold voltage during the conversion process
- (C) stabilize the input analog signal during the conversion process
- (D) sample and hold the D/A converter staircase waveform during the conversion process
- (ii) A log amplifier has _____ in the feedback loop.
- (A) A diode (B) A BJT
- (C) A Resistor (D) Either a diode or a BJT

- (iii) Root locus specifies the movement of closed loop poles especially when the gain of system_____.
- (A) Remains constant (B) Exhibit variations
(C) Gives zero feedback (D) Gives infinite poles
- (iv) How is the sinusoidal transfer function obtained from the system transfer function in frequency domain in pole-zero diagram ?
- (A) Replacement of 'j ω ' by 's'
(B) Replacement of 's' by 'j ω '
(C) Replacement of 's' by ' ω '
(D) Replacement of ' ω ' by 's'
- (v) In class C operation the Q point on dc load line is located
- (A) approximately at the centre
(B) near cut off
(C) beyond cut off
(D) between cut off and centre
- (vi) In an amplifying system a power amplifier forms the
- (A) input stage (B) intermediate stage
(C) output stage (D) dc power supply
- (vii) Which of the following statement/ statements is/ are correct for an Op-amp ?
- (i) Its open loop gain is very high.
(ii) It is a non-linear circuit.
- (A) (i) only (B) (ii) only
(C) (i) and (ii) both (D) None
- (viii) Input for an oscillator circuit is obtained from
- (A) an external source (B) a feedback network
(C) an amplifier (D) None
-

