

Instructions: All questions in **Section – I** carry equal marks.
 Attempt any **Three** questions in **Section – I**.
 Questions in **Section – II** is **COMPULSORY**.

Section – I

- Q-I A. What are the voltage limiters? Why it is necessary? Describe inverting comparator with negative voltage limiting using suitable diagram. 7
 B. Explain working of the ON/OFF temperature controller designed using LM339 with necessary circuit diagram. 7
- Q-II A. Draw the circuit diagram of a level detector for photo diode using IC LM311 and discuss its working briefly. 7
 B. Explain working of the LM380 power amplifier with suitable circuit and pin diagram. Write its applications. 7
- Q-III A. Discuss IC8038 function generator with neat and clean diagram. Write its important features. 7
 B. Draw pin diagram of IC9400. Using this IC explain frequency to voltage converter and state its design and calibration method. 7
- Q-IV A. How triangular wave generator and sawtooth wave generator are differentiated with each other? Draw the circuit diagram of sawtooth wave generator using OPAMP and explain its working. 7
 B. Discuss the working of the Wein bridge oscillator using OPAMP with necessary circuit diagram. Obtain the expression for its frequency of oscillations. Using IC741, design a Wein bridge oscillator of frequency 5 KHz. 7
- Q-V A. Design and draw the circuit diagram of a second order low pass Butterworth filter using IC 741 for a higher cut off frequency of 1 KHz and gain of 1.59. 7
 B. Design and draw the circuit diagram of a 60 Hz active Notch filter using Twin-T network. 7
- Q-VI A. Design and draw the circuit diagram of a wide band pass filter with $f_L=200\text{Hz}$ and $f_H = 1 \text{ KHz}$ with band pass gain of 4 (use IC 741) 7
 B. What is Universal filter IC FLT-U2? Using FLT-U2, design a second order inverting Butterworth band pass filter with centre frequency of 5 KHz and $Q=10$. 7

N 281-2

- Q-VII A. What are graphic equalizers? Give its circuit and draw its response. 7
Where are these used?
- B. List main features of Norton's OPAMP ? Draw and discuss the circuit of 7
AC coupled inverting amplifier using Norton OPAMP.
- Q-VIII A. What is meant by active tone controls? Draw circuit diagram and explain 7
working of any active tone control circuit.
- B. What are the requirements of Video amplifier? Discuss wide banding 7
technique in Video amplifiers using compounding of devices.

Q-IX MCQs

8

1. A Schmitt trigger is
 - A. a comparator with only one trigger point.
 - B. a comparator with three trigger points.
 - C. a comparator with hysteresis.
 - D. a comparator with no trigger points.

2. How to limit the output voltage swing only to positive direction in voltage limiter circuit?
 - A. Combination of two Zener diodes
 - B. Combination of Zener and rectifier diodes
 - C. Combination of two rectifier diodes
 - D. Combination of two rectifier diodes and two Zener diodes

3. To a Schmitt trigger in inverting configuration an input sine wave of $2V_p$ is applied. What will be the output waveform, if the upper and lower threshold voltages are $0.5V$?
 - A. Pulse waveform
 - B. Sawtooth waveform
 - C. Square waveform
 - D. Triangular waveform

4. Which one waveform is denoted as 'sweep' ?
 - A. Sawtooth waveform
 - B. Sinusoidal waveform
 - C. Square waveform
 - D. Square waveform

5. Which one is the characteristics of a Butterworth filter
 - A. Flat pass band & flat stop band
 - B. Rippled pass band & flat stop band
 - C. Flat pass band & rippled stop band
 - D. Rippled pass band & rippled stop band

6. For Uncommitted OPAMP section of FLT-U2 , mark the WRONG statement.
 - A. It can be used both as gain stage and a Buffer amplifier
 - B. It can be used to raise order of low pass and high pass filter functions
 - C. It can not be used to realize NOTCH filter and ALL PASS filter.
 - D. It can be used to raise order of band pass filter function.

7. Which one is the WORNG statement for FET input stage OPAMP
 - A. Very high input impedance
 - B. Very High slew rate
 - C. High bias current
 - D. High CMRR

8. LF155/156/157 series are which type of ICs
 - A. Nortons OPAMP IC
 - B. Video Amplifier IC
 - C. FET input OPAMP IC
 - D. Switched Capacitor Filter IC