

M.Sc Sem-3 Examination

502

Physics

Time : 2-30 Hours]

November-2024

[Max. Marks : 70

- Q.1 (A) Explain Picard's method of solving ordinary differential equation. Using this method, solve $\frac{dy}{dx} = -xy$ with $x_0 = 0, y_0 = 1$ upto third approximation. [07]
- (B) Write merits and demerits of Adams-Bashforth Method. If $\frac{dy}{dx} = 2e^x y$, $y(0)=2$, find $y(4)$ using Adams predictor correction formula by calculating $y(1)$, $y(2)$ and $y(3)$ using Euler's modified formula. [07]

OR

- Q.1 (A) Write briefly about Runge-Kutta (RK) method for solving ordinary differential equations. Using 4th order RK method to find an approximate value of y when $x = 0.2$ given that $\frac{dy}{dx} = x + y$ and $y = 1$ when $x = 0$. [07]
- (B) How are Euler's method and its modified form found helpful for solving the ordinary differential equation? explain with their limitations. [07]
- Q.2 (A) Solve the Poisson equation $u_{xx} + u_{yy} = -81xy$, $0 < x < 1$, $0 < y < 1$ given that $u(0,y)=0$, $u(x,0)=0$, $u(1,y)=100$, $u(x,1)=100$ and $h=1/3$. [07]
- (B) Calculate the equation $\frac{\partial u}{\partial t} = \frac{\partial^2 u}{\partial x^2}$ subject to the conditions $u(x, 0) = \sin \pi x$, $0 \leq x \leq 1$; $u(0,t)=u(1,t)=0$, using (a) Schmidt method, (b) Crank-Nicolson method and (c) Du Fort-Frankel method. Carryout computations for two levels, taking $h=1/3$ and $k=1/36$. [07]

OR

- Q.2 (A) Solve the elliptic equation $u_{xx} + u_{yy} = 0$ for the following square mesh with boundary values as shown. [07]

	0	300	600	300	0	0
500		u_1	C	u_2	u_3	500
1000	A	u_4		u_5	u_6	B 1000
500		u_7		u_8	u_9	500
0						0
0	0	300	600	300	0	

- (B) Solve the equation $\frac{\partial u}{\partial t} = \frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2}$ satisfying the initial condition: $u(x, y, 0) = \cos 2\pi x \cos 2\pi y$, $0 \leq x, y \leq 1$ and conditions: $u(x, y, t) = 0$, $t > 0$ on the boundaries, using Alternating Direction Explicit (ADE) method with $h = \frac{1}{3}$ and $\alpha = \frac{1}{8}$. Calculate the results for one-time level. [07]
- Q.3 (A) Explain the working of 32-bit diode ROM organized as 8 words of 4 bit each, drawing necessary circuit diagram. Write Boolean equations for Y_0 , Y_1 , Y_2 and Y_3 . [07]

- (B) Draw the circuit diagram of Monostable multivibrator using IC-555 and explain the working of the circuit. [07]

OR

- Q.3 (A) Draw the block diagram for serial-input, serial-output shift register using IC-74LS91 and explain its working. [07]

- (B) Draw the circuit diagram of Switched tail Counter and its truth table to explain its working. [07]

- Q.4 (A) Explain the working of D/A converter drawing necessary circuit diagram with Read input, Flip-Flops, level amplifiers and the D/A converter. [07]

- (B) Discuss the working of 3-bit A/D converter using simultaneous conversion method, drawing necessary block diagram. [07]

OR

- Q.4 (A) Explain the D/A conversion Accuracy and Resolution. [07]

- (B) Discuss the working of A/D conversion using Successive Counter, drawing necessary block diagram. [07]

- Q.5 Answer in brief **Any Seven** questions from the following: [14]
(Each question is of **two** marks).

- (i) State multi-step methods of solving the differential equation?
- (ii) State limitations of Picard's method of solving the ordinary differential equation.
- (iii) In Euler's method, if 'h' is small the method is too slow, if 'h' is large, it gives inaccurate value. (TRUE or FALSE)
- (iv) Write an expression of standard 5-point formula of partial differential equations.
- (v) What is the classification of the partial differential equation $f_{xx} + 2f_{xy} + f_{yy} = 0$?
- (vi) Why is Crank-Nicholson's scheme called an implicit scheme?
- (vii) Assuming that the input reference voltage is $V = 10.0$ V dc, the digital output of the 8-bit simultaneous A/D converter for an input voltage of 6.40 V is _____.
- (viii) A TTL clock circuit provides a 10-MHz clock frequency with a stability better than 10 parts per million (ppm) over a 24-h time period. What are the frequency limits of the clock?
- (ix) The output voltage caused by 11100 in a 5-bit ladder is _____.
The input levels are 0 = 0 V and 1 = +10 V?
- (x) The output voltage caused by 4th bit in a 5-bit ladder is _____.
The input levels are 0 = 0 V and 1 = +5 V?
- (xi) The maximum clock frequency that can be used with a logic gate having a propagation delay of 200 ns, is _____.
- (xii) Find the binary equivalent weight of each bit in a 4-bit system.

*** PAPER ENDS ***