

B.Sc. Sem.-3 Examination
Ele-202
Electronics

Time : 2-30 Hours]

October 2024

[Max. Marks : 70]

Instructions : (1) All questions carry equal marks.
 (2) Symbols carry their usual meaning.

1 (a) Explain transformation of impedances with tapped resonant circuits. 7
 (b) Explain reactance T networks for impedance transformation in detail. 7

OR

1 (a) Explain tapped anti resonance circuit for impedance transformation with equation. 7
 (b) Discuss two mesh coupled circuit used for impedance transformation. 7

2 (a) Explain how a high pass RC circuits behave as differentiator. 7
 (b) Derive the relation between neper & decibel. 7

OR

2 (a) Derive the equation of characteristic impedance of symmetrical networks. 7
 (b) Discuss the current & voltage ratio as exponentials in filters. 7

3 (a) Explain half adder & full adder with the help of truth-table. 7
 (b) Discuss in detail about Arithmetic logic unit. 7

OR

3 (a) Explain how 555 timer can be used as Astable Multivibrator. 7
 (b) Explain how 555 timer can be used as Monostable Multivibrator. 7

4 (a) Explain Large computers, Medium-size computers & Microcomputers in detail. 7
 (b) Explain Machine language, assembly language & high level language. 7

OR

4 (a) Explain 8085 hardware & programming model in detail. 7
 (b) Explain data transfer, Arithmetic, logical, branch & machine control instructions. 7

5 Attempt any seven out of twelve : 14

- (1) What is impedance? What is resonance?
- (2) Write Weber - Fechner Law
- (3) Co-efficient of coupling $k = \dots$ & Ideal transformer is assume to have losses.
- (4) 1 neper = dB & 10 neper = dB.
- (5) Draw integrator & differentiator circuit.
- (6) The bel is defined as logarithm of a ratio.
- (7) What is ALU?
- (8) Define duty cycle.
- (9) Define Multivibrator.
- (10) List flags of 8085.
- (11) Give the full form of ASCII & MSI.
- (12) Define operating system.