

B.Sc. Sem.-2 (NEP) Examination

DSC-C-ELE-121 (T)

Electronics

(History of Indian Satelite Network, Electric Device & Digital)

Time : 2-00 Hours]

April 2024

[Max. Marks : 50]

Instructions : (1) Figures to the right indicate Full Marks of the questions.

(2) Symbol used their usual meaning.

1 Draw the block diagram of typical Earth station & explain Fixed satelite service in detail. 10

OR

Draw the INSAT frequency plan & explain INSAT in detail.

2 Explain about Norton's theorem & Maximum power transfer theorem in detail. 10

OR

State & explain Kirchhoff's voltage law in detail. Also discuss Ideal constant voltage source.

3 Explain how zener diode works as voltage regulator. Also discuss how zener diode works as peak cliper. 10

OR

Draw the symbol of LED & discuss its construction, working & application.

4 $\underline{Y} = F(A, B, C) = \sum m(3, 5, 6, 7)$ 10

OR

Explain 7 segment decoder & Ex - OR gate in detail.

5 Attempt any ten out of twelve : 14

- (1) Name two distinct parts of satelite system.
- (2) The satelite revolves round the Earth at altitude of km over the equator.
- (3) In satelite communication modulation is used.
- (4) Generally current leaving from the network is taken as
- (5) The superposition theorem is essentially based on the concept of
- (6) An ideal constant current source has resistance.
- (7) Draw the symbol of Tunnel diode.
- (8) A varacter diode is always biased.
- (9) PIN diode is composed of section.
- (10) What is overlapping in K-Map?
- (11) What is Rolling in K-Map?
- (12) Give the full form of ROM.