

B.Sc. Sem.-1 Examination

DSC-C-111

Electronics

Time : 2-00 Hours]

February 2025

[Max. Marks : 50

- Instructions :** (1) All questions are compulsory.
 (2) All questions carry equal marks.
 (3) Symbol used have their usual meaning.

- 1 Give the colour code for carbon resistance & discuss any two types of resistor in detail 10
 OR
 Explain about fixed type & variable types of capacitors in detail. Also discuss energy stored in capacitor.
- 2 Explain about Binary to Gray, Gray to Binary & Excess-3 code in detail. 10
 OR
 (a) $347B.5C_{(16)} = \dots\dots\dots (10) = \dots\dots\dots (2)$
 (b) $749.56_{(10)} = \dots\dots\dots (16) = \dots\dots\dots (2)$
 (c) $342.41_{(10)} = \dots\dots\dots (8)$
- 3 Explain about the construction, working, V/I characteristics, parameters & application of PN Junction diode. 10
 OR
 Explain about clipper & clamper circuit in detail.
- 4 Explain about CB, CC & CE configuration of a transistor. Also discuss transistor as an amplifier. 10
 OR
 Discuss the characteristics of common base & common emitter circuit.
- 5 Answer in short (Any ten) : 10
 (1) $3.2 \text{ M } \Omega = \dots\dots\dots \text{ k } \Omega$
 (2) $4.7 \text{ micro farad} = \dots\dots\dots \text{ nano farad}$
 (3) What is the unit of inductor?
 (4) Give the full form of ASCII.
 (5) What is the base of Hexa decimal number system?
 (6) $A+B = \dots\dots\dots$
 (7) Draw the symbol of PN Junction diode.
 (8) Define : Clipper.
 (9) Define : Clamper.
 (10) Draw the symbol of PNP transistor.
 (11) Give the full form of BJT
 (12) In which configuration transistor works as an amplifier?