

2/161

1801E1191

Candidate's Seat No : _____

IMSc CS (NEP) Sem.-1 Examination

Digital Electronics for CS

Time : 2-00 Hours]

January-2025

Marks:25

Q. 1 (A) EACH QUESTION CARRIES 3MARKS

[06]

- i) Prove De Morgan's law using perfect induction method.
ii) Simplify the given Boolean equation **using basic Boolean laws** and draw the simplified gated circuit daigram. (e.g. A' represents complement of A)
 $Y = A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD' + A'BCD + A'BCD' + ABC'D + ABCD$

(B) EACH QUESTION CARRIES 2MARKS

[04]

- i) Explain universal gates with symbols and truth tables.
ii) Explain basic duality of Boolean algebra.

OR

Q. 1 (A) EACH QUESTION CARRIES 3MARKS

[06]

- i) Simplify the given Boolean equation **using Karnaugh map** and draw the simplified gated circuit diagram using AND-OR network.

$$Y = m_2 + m_5 + m_7 + m_9 + m_{11} + m_{13}$$

$$d = m_0 + m_8 + m_{10} + m_{14} \text{ (Don't cares)}$$

- ii) Simplify the given Boolean equation **using Karnaugh map** and draw the simplified gated circuit diagram using OR-AND network.

$$Y = m_3 + m_8 + m_9 + m_{11} + m_{14} + m_{15}$$

$$d = m_2 + m_7 + m_{12} + m_{13} \text{ (Don't cares)}$$

(B) EACH QUESTION CARRIES 2MARKS

[04]

- i) Write the truth table of 3-bit X-OR and X-NOR gate.
ii) Write associative and distributive law for Boolean algebra.

Q. 2

- (A) Write basic steps for binary multiplication for generalized parallel arithmetic element and explain using appropriate example.

[06]

(B) EACH QUESTION CARRIES 2MARKS

[04]

- i) Make the JK flip flop using RS flip flop and explain its truth table.
ii) Draw the circuit diagram of BCD counter.

OR

(P.T.O)

Q. 2

(A) Write basic steps for binary division for generalized parallel arithmetic element and explain using appropriate example. [06]

(B) EACH QUESTION CARRIES 2MARKS [04]

- i) Make a full adder using two half adders.
- ii) Draw the block diagram and gated diagram of master slave flip flop.

Q.3 EACH QUESTION CARRIES 1 MARK (ATTEMPT ANY FIVE) [05]

- i) What is cycle stealing in DMA?
 - ii) Write the difference between PROM and EPROM.
 - iii) Draw the circuit diagram of NAND gate decoder.
 - iv) Write an example of zero address instruction.
 - v) How many select lines require in 16 to 1-line multiplexer.
 - vi) Write full form of ASCII.
 - vii) Explain importance of clock in digital circuit.
-