

## B.Sc. Sem.-5 Examination

CC-303

Electronics

March-2025

Time : 2-30 Hours]

[Max. Marks : 70

Instructions: (1) Symbols used here have their usual meanings.  
(2) Figures to the right indicate marks.

- Q-1 (i) Explain working principle of chopper type micro-voltmeter. (7)  
(ii) Explain True RMS voltmeter in brief. (7)
- OR
- Q-1 (i) Explain the working of the Transistor Voltmeter with suitable circuit diagram. (7)  
(ii) Explain the basic principle of the differential voltmeter. (7)
- Q-2 (i) Draw block diagram of ramp type DVM. Explain function of each block. (7)  
(ii) Write a short-note on integrating type DVM. (7)
- OR
- Q-2 (i) A 4 and  $\frac{1}{2}$  digit voltmeter is used for voltage measurements. (1) Find its resolution (2) How would 12.98 V be displayed on 10 V range? (3) How would 0.6973 be displayed on 1 V and 10 V ranges. (7)  
(ii) Explain the basic principle of successive approximation type DVM. (7)
- Q-3 (i) Draw the block diagram of C.R.O. Explain function of each block briefly. (7)  
(ii) Write a short note on CRT circuits. (7)
- OR
- Q-3 (i) Explain construction of distributed parameter delay line in detail. (7)  
(ii) Write a note on "Graticules" of the CRT. (7)
- Q-4 (i) With the help of suitable diagram, explain pulse terms/characteristics (1) rise time (2) fall-time (3) duty cycle (4) sag (7)  
(ii) Draw the block diagram of general purpose pulse generator providing negative pulses of variable frequency, duty cycle and amplitude. (7)
- OR
- Q-4 (i) Briefly explain the role of astable multivibrator in pulse and square-wave generation. (7)  
(ii) Explain basic concept of simplified current source operation in laboratory pulse generator. (7)
- Q-5 Attempt any seven out of twelve. (14)
- (1) What is full form of PMMC?
  - (2) Mention any one limitation of a Transistor Volt Meter?
  - (3) Mention different modes of a DC standard volt-meter .
  - (4) What do you mean by 3  $\frac{1}{2}$  digit DVM?
  - (5) What is the resolution of a 3  $\frac{1}{2}$  digit display on 1 V?
  - (6) Define Sensitivity of digital meters.
  - (7) Write the full form of C.R.O.
  - (8) What is the function of Delay Line of C.R.O.?
  - (9) Where phosphor is used in CRT? Why?
  - (10) Define : Duty cycle.
  - (11) Write any one common characteristic of a signal generator.
  - (12) Draw the block diagram of a simple sine-wave generator.