

MSc Sem.-2 Examination**409****Medical Physics****May-2025****Time : 2-30 Hours]****[Max. Marks : 70**

- Q.1** (A) Explain the construction and working of an NPN Bipolar Junction Transistor (BJT) in common-emitter configuration. Sketch and explain its I-V characteristics in different regions of operation. [07]
- (B) What are the essential components of a regulated DC power supply? Define line regulation and load regulation. Explain their significance in power electronics. [07]

OR

- Q.1** (A) Describe the structure and working of a Light Emitting Diode (LED). Explain how the color of the emitted light is determined. [07]
- (B) What is a DC-DC converter? Explain the working principle of a buck or boost converter and discuss applications in RF power supplies. [07]
- Q.2** (A) Explain the concept of feedback in electronic circuits. Differentiate between positive and negative feedback with suitable circuit examples. How does feedback influence gain, bandwidth, and stability of an amplifier? [07]
- (B) State and explain the Barkhausen criterion for sustained oscillations. Derive the condition for oscillation in a general feedback oscillator circuit using loop gain analysis. [07]

OR

- Q.2** (A) Draw and explain the Wien-bridge oscillator circuit. Derive the condition for oscillation and expression for frequency. How is amplitude stabilization achieved in practical circuits? [07]
- (B) Explain the construction and working of a UJT relaxation oscillator. Derive an expression for its frequency of oscillation. Why is it suitable for sawtooth waveform generation? [07]
- Q.3** (A) Describe the structure and working of a differential amplifier. Explain the roles of inverting and non-inverting inputs. Discuss common-mode and differential-mode operation with appropriate equations. [07]
- (B) Describe and derive the operation of Voltage-to-Current (V-I) and Current-to-Voltage (I-V) converters using op-amps. Mention typical scenarios where each is used. [07]

OR

- Q.3** (A) Discuss the working of a logarithmic amplifier using an op-amp and diode. Derive the expression for the output voltage and mention practical applications. [07]

- (B) How can op-amps be used to build function generators? Explain with circuits for generating square, triangle, and sine waveforms. [07]
- Q.4** (A) Draw logic symbols of OR, AND, NOT, NOR, and NAND gates, and write truth table of each gate [07]
- (B) Give classification of the 8085 Microprocess instructions and discuss each with relevant example [07]

OR

- Q.4** (A) Draw circuit diagram of R-S and J-K flip-flops and explain working of each one with their truth tables [07]
- (B) Give brief introduction of 8085 Microprocessor: Draw INTEL 8085 pinout diagram and discuss it. [07]
- Q.5** Answer in brief **Any Seven** questions from the following: (Each question is of **two** mark). [14]
- (i) Why is MOSFET preferred in digital circuits?
 - (ii) Compare tunnel diode and conventional diode in terms of doping and I-V characteristics.
 - (iii) Name one advantage of SMPS over linear power supplies.
 - (iv) Why are LC oscillators unsuitable for low-frequency applications?
 - (v) Why is a three-stage RC network used in a phase-shift oscillator?
 - (vi) What is a varactor diode and how is it used in a tuned oscillator? Write its applications.
 - (vii) List ideal characteristics of an operational amplifier.
 - (viii) What is the voltage gain expression for an inverting amplifier?
 - (ix) What is an active filter? Name two types of active filters.
 - (x) Write name of general-purpose registers of INTEL 8085 MPU
 - (xi) What is function of address bus?
 - (xii) How many flags are there in 8085 MPU?

***** PAPER ENDS *****