

DD-113

December-2013

5 Years M.Sc. (CA & IT) Integrated (KS) 1st Sem. FY M.Sc.

Fundamentals of Computer Organization


Time : 3 Hours]

[Max. Marks : 100

- Instructions :**
- (1) All questions are compulsory.
 - (2) Draw diagrams wherever necessary.
 - (3) Only simple calculators are allowed.

1. (a) Solve any **five** : (2 marks each) **10**
 - (1) Convert 131.5625 into Binary number.
 - (2) Convert 1011011.001101 in to decimal number.
 - (3) Perform multiplication of 16×2.75 in binary number.
 - (4) Perform subtraction of $110 - 0.111$ using 1's compliment.
 - (5) Convert B6C7 in to decimal number.
 - (6) Convert 110110.011 into Octal number.
- (b) Explain Error detection method with parity using circuit diagram. **5**
- (c) Explain mantissa, exponent, normalization with examples in floating point representation. **5**

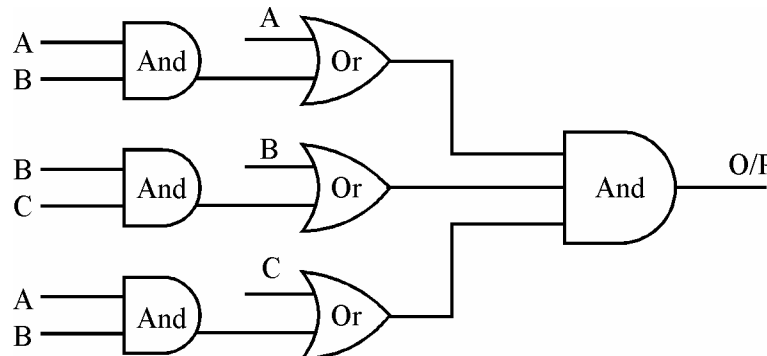2. (a) What are universal gate ? Prove that NAND and NOR gates are universal gates. **5**
- (b) Explain Exclusive OR and Exclusive NOR gate with truth table, symbol and diagram. **3**
- (c) Explain Duality with example. **3**
- (d) Write and prove De.Morgan's theorem with Boolean expression and diagrams. **5**
- (e) Write the Boolean expression for the logic diagram given below and simplify it as much as possible. Also draw the circuit of simplified expression. **4**



3. (a) Explain Binary Adder-Subtractor with circuit diagram. **5**
- (b) Explain four input multiplexer with circuit and block diagram. **5**
- (c) Explain full adder with diagram. **5**
- (d) What are decoders ? Explain 3 to 8 decoders with truth table and block diagram. **5**
4. (a) What are printers ? List various type of printers and explain working of any three. **5**
- (b) What is Asynchronous data transfer ? Explain handshaking method of asynchronous data transfer. **5**
- (c) Write short note on DMA. **3**
- (d) Write short note on Magnetic Disk. **3**
- (e) Explain : (1 marks each) **4**
- (1) DRAM
- (2) EEPROM
- (3) OCR
- (4) MICR
5. (a) Explain the working of SR flip-flop. List various flip-flops and define flip-flop. **5**
- (b) Explain Asynchronous binary counter with circuit and clock diagram. **5**
- (c) Explain various type of instruction formats. **5**
- (d) Reduce following expression using K-Map and implement the real minimal expression in both SOP and POS. Decide which is minimal expression. **5**
- $$f = \sum (0, 2, 4, 6, 7, 8, 10, 12, 13, 15)$$
-