

Seat No. : _____

AX-102

May-2016

B.Sc., Sem.-II

CC-103 : Electronics

Time : 3 Hours]

[Max. Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Symbols have their own meaning.

1. (a) Discuss the characteristics of CB circuit. **7**
OR
Discuss the characteristics of CE circuit.
- (b) Define stability. Draw a circuit of fixed bias and obtain stability factor S. **7**
OR
Draw a circuit diagram of collector to base bias and obtain stability factor S.
2. (a) Considering a transistor as a 4 terminal active network, define and explain the hybrid or h parameters. Also draw and explain the h parameter equivalent circuit. **10**
OR
- (i) Draw the ac equivalent circuit of a CE amplifier and find the equations for voltage gain and power gain. **5**
- (ii) In a transistor amplifier, when signal changes by 0.04 V, I_B changes by 20 mA & I_C changes by 2 mA. If $R_C = 5 \text{ k}\Omega$ & $R_L = 10 \text{ k}\Omega$, find current gain, input impedance, ac load, voltage gain and power gain. **5**
- (b) Give comparison of CB, CC & CE amplifier. **4**
OR
Define :
(1) Z parameter
(2) Y parameter **4**
3. (a) State and prove reciprocity theorem. **7**
OR
Give conversion between T network to π network and π network to T network. **7**

- (b) Explain parallel resonance circuit and derive the expression of resonance frequency. 7

OR

What is bandwidth ? Obtain the equation of bandwidth $\Delta f = \frac{f_r}{Q}$ in the series resonance circuit. 7

4. (a) Explain don't care condition. Reduce the logic equation $F(A, B, C, D) = \Sigma m(2, 3, 7) + d(10, 11, 12, 13, 14, 15)$ by using K-map. 7

OR

You are given the following Boolean equation $Y = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D}$. Show the simplified NAND-NAND circuit for this. Also show the simplified NOR-NOR circuit.

- (b) Write notes on (any **one**) : 7
- (i) Seven segment decoder
 - (ii) Multiplexer

5. Answer in short : 14

- (1) Draw the symbol for NPN transistor.
 - (2) In which configuration amplifier has highest voltage gain ?
 - (3) Obtain the relation between β & α .
 - (4) What is equivalent network ?
 - (5) Define impedance.
 - (6) Define potential source.
 - (7) What is an active region ?
 - (8) Define Q.
 - (9) Give the statement of maximum power transfer theorem.
 - (10) Define : Decoder
 - (11) Define Demultiplexer.
 - (12) What is ROM ?
 - (13) What is overlapping in K-map ?
 - (14) How does EX-OR gate differ from OR gate ?
-