

# LE-105

April-2014

B.Sc. (Sem.-VI)

## CC-308 : ELECTRONICS

Time : 3 Hours]

[Max. Marks : 70

1. (a) (i) Explain 4-bit binary ladder and derive the equation for output voltage. **10**  
(ii) Draw the binary ladder with a digital input of 0100.

**OR**

- (i) Explain counter type A/D converter.  
(ii) How does the continuous – type A/D converter differ from the counter-type A/D converter ?
- (b) With illustration explain monotonicity test. **4**

**OR**

Draw the circuit diagram of dual – slope A/D converter.

2. (a) Giving flowchart writes instructions to set up time delays, using one register, a register pair and a loop-within-a-loop techniques. **10**

**OR**

With flowchart and delay calculations, write a program to construct a Zero-to-Nine counter. Assume the clock frequency is 2 MHz.

- (b) Give the instructions and delay calculations of a hexadecimal counter of a system with a  $0.5\mu\text{s}$  clock period. Use register C to set up a two millisecond delay between each count. **4**

**OR**

Write a program to turn a light on and off every 10 seconds.

3. (a) Give and explain with illustration, the instructions required for the execution of stack. **9**

**OR**

Illustrate how information is exchanged between the program counter and the stack and identify the contents of the stack pointer register when a subroutine is called.

- (b) Explain : Conditional call and Return instruction. **5**

**OR**

- (i) Draw flowchart for the traffic signal controller.  
(ii) Give the block diagram of multiple-calling for a subroutine.

4. (a) Explain 8255A general-purpose programmable devices, compatible with any microprocessor. **10**

**OR**

Explain DAC 0808 giving its features, pin configuration, block diagram and typical applications.

- (b) Write a note on Mode 0 and BSR Mode. **4**

**OR**

Write a program to generate square wave.

5. Do as directed : **14**

- (1) What is the LSB weight of a 8-bit resistive ladder ?
- (2) How many comparators are required to build a 5-bit simultaneous A/D converter.
- (3) What do you understand by SAR ?
- (4) What is the greatest weakness of a single-ramp A/D converter ?
- (5) Give full form of instruction RAR.
- (6) Define : counter.
- (7) Accuracy of the time delay depends on the accuracy of \_\_\_\_\_.
- (8) What RST instruction does ?
- (9) A stack is a \_\_\_\_\_ - bit register.
- (10) 8085 instruction set includes \_\_\_\_\_ Restart instructions.
- (11) Define : Setting time of DAC.
- (12) How many bits are required in a DAC to get a resolution of 1 mv, if full scale output voltage is 10V ?
- (13) What is the resolution of a 10-bit DAC ?
- (14) Give the name of two programmable devices of Intel family.

\_\_\_\_\_