

Seat No. : _____

JF-114

January-2021

B.C.A., Sem.-III

**CC-201 : Computer Organization
(New Course)**

Time : 2 Hours]

[Max. Marks : 50

- Instructions :** (1) All Questions in **Section I** carry equal marks.
(2) Attempt any **TWO** questions in **Section I**.
(3) Question **5** in **Section II** is **COMPULSORY**.

Section – I

1. (A) List the different types of Gate, explain all in detail with diagram and Truth Table. **10**
(B) List the different types of Flip-Flops. Explain JK Flip-flop and T Flip-flop in detail. **10**
2. (A) Explain Bus Memory Transfer in detail with diagram. **10**
(B) Explain Binary Adder and Binary Adder Subtractor in detail. **10**
3. (A) Explain Common Bus System in detail with diagram. **10**
(B) List the different types of Addressing Modes. Explain Immediate, Direct, Indirect and Register Indirect mode in detail. **10**
4. (A) Explain I/O Bus System, Isolated and Memory-Mapped I/O in detail. **10**
(B) Explain Cache Memory, Main Memory and Associative Memory from Memory Hierarchy. **10**

Section – II

5. Answers the following questions : (any 5 × 2 marks each) 10
- (1) _____ is called Universal Gate.
(a) NOT (b) AND
(c) NAND (d) EX-OR
 - (2) Full Adder require minimum Two Hal Adder. (True/False)
 - (3) In _____ combinational circuit has n input lines and maximum 2^n output line.
(a) Decoder (b) Multiplexer
(c) Encoder (d) Full Adder
 - (4) Full form of RTL.
 - (5) Convert 456_{10} into 10's complement.
 - (6) Operand is store in _____ part.
(a) Accumulator (b) Memory Adders
(c) Bus (d) All of the above
 - (7) Cache Memory is fastest memory in computer system. (True/False)
 - (8) DMA transfers are performed by _____ circuit.
(a) Data Controller (b) Device Controller
(c) DMA Controller (d) All of the above
 - (9) Flip-flop store one bit of data. (True/False)
 - (10) Bus system is used three state gates. (True/False)
-