

B.Sc Sem.-3 Examination

CC 202

Electronics

Time : 2-00 Hours]

January 2021

[Max. Marks : 50

SECTION - I

- Q.I (A) Explain Transformation of impedances with tapped resonant circuits. 7
(B) Explain ideal transformer with mesh impedances, ratio of currents and voltage. 7
- Q.II (A) Discuss reactance L-section for impedance transformation. Derive its equation for $R < R_p$. 7
(B) Explain magnetically coupled circuit. Derive its coefficient of coupling. 7
- Q.III (A) Explain how a low pass RC circuit behaves as an integrator. 7
(B) Derive the equation of characteristic impedance of symmetrical networks. 7
- Q.IV (A) Explain how a high pass RC circuit behaves as differentiator. 7
(B) Derive the relation between neper and decibel. 7
- Q.V (A) Draw full adder and explain it with the help of Truth table and karnaugh map. 7
(B) Explain how 555 timer can be used as monostable multivibrator. 7
- Q.VI (A) Draw & explain binary adder-subtractor with the help of example. 7
(B) Discuss the Schmitt trigger operation of the 555 timer. 7
- Q.VII (A) Explain Machine language, assembly language & high-level language. 7
(B) Explain 8085 hardware and programming model in detail. 7
- Q.VIII (A) Explain large computers, medium-size computers & microcomputers. 7
(B) Write instructions to load the 43H & 03H in register A & B respectively. Add the numbers. and display the sum at the LED output port PORT 1. 7

SECTION - II

- Q.IX Attempt any EIGHT 8
- (A) Ideal transformer is assumed to have value of $k =$ _____.
- (B) The value of anti-resonant resistance is dependent on the _____ ratio chosen for the circuit.
- (C) For values of k/k_c greater than _____, the circuit is over-coupled.
- (D) Coefficient of coupling $k =$ _____.
- (E) For better differentiation CR should be as _____ as possible.
- (F) The bel is defined as the _____ of a power ratio.
- (G) 10 neper = _____ db.
- (H) The loudness L may be expressed as $L =$ _____.
- (I) In half adder, if $A=1$ and $B=1$ then $SUM =$ _____.
- (J) In full adder, output of XOR gate is called _____.
- (K) The output of the AND gate in half adder circuit is called _____.
- (L) Pin number 5 of 555 timer is called _____.
- (M) A set of instructions written for the microprocessor to perform a task is called a _____.
- (N) Programming languages that are intended to be machine-independent are called _____.
- (O) The Zero flag is set to 1 when the result is _____.
- (P) The Sign flag is set if bit D7 of the result is _____.